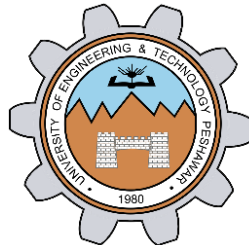


**DECODERS IN
VERILOG**

LAB # 08



Fall 2023

CSE-304L


Computer Organization & Architecture Lab

Submitted by: **AIMAL KHAN**

Registration No.: **21PWCSE1996**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: 

Submitted to:

Dr. Bilal Habib

Sunday, December 17, 2023

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown [Marks0] [Marks 0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
Total Marks Obtained: _____ Instructor Signature: _____				

Decoders in Verilog

Objectives:

- Create and test various decoders in Verilog.

Tasks:

Task 1: Implement 2X4 Decoder using gate level modeling in Verilog.

DUT Code:

```
module Decoder_2x4(A, B, E, I);  
  
    input A, B, E;  
    output [3: 0]I; // 3 inputs  
  
    wire nA, nB;  
  
    not n1(nA, A);  
    not n2(nB, B);  
  
    and a1(I[0], nA, nB, E);  
    and a2(I[1], nA, B, E);  
    and a3(I[2], A, nB, E);  
    and a4(I[3], A, B, E);  
endmodule;
```

Test Code:

```
module Decoder_2x4_tb;  
  
    reg A, B, E;  
    wire [3:0] I;  
  
    // Instantiate the Decoder_2x4 module  
    Decoder_2x4 uut (  
        .A(A),  
        .B(B),  
        .E(E),  
        .I(I)  
    );  
  
    // Clock generation (not used in this example)  
    reg clk = 0;  
    always #5 clk = ~clk;  
  
    // Testbench stimulus  
    initial begin  
        // Test case 1: Enable (E) is high, A=0, B=0  
        A = 0;  
        B = 0;
```

```

        E = 1;
        #10 $display("Input: A=%b, B=%b, E=%b, Output: I=%b", A, B,
E, I);

        // Test case 2: Enable (E) is high, A=1, B=0
        A = 1;
        B = 0;
        #10 $display("Input: A=%b, B=%b, E=%b, Output: I=%b", A, B,
E, I);

        // Test case 3: Enable (E) is high, A=0, B=1
        A = 0;
        B = 1;
        #10 $display("Input: A=%b, B=%b, E=%b, Output: I=%b", A, B,
E, I);


        // Test case 4: Enable (E) is high, A=1, B=1
        A = 1;
        B = 1;
        #10 $display("Input: A=%b, B=%b, E=%b, Output: I=%b", A, B,
E, I);

        // End simulation
        $finish;

end
endmodule;

```

Output:

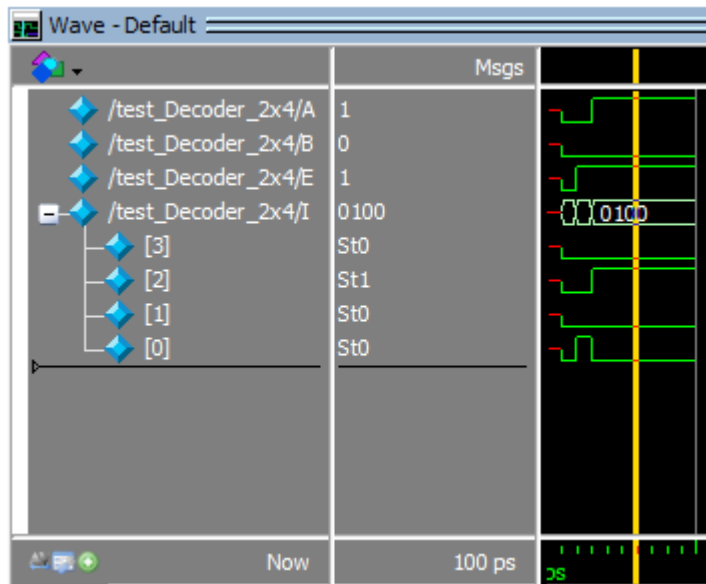

Task 2: Implement 3X8 Decoder using gate level modeling in Verilog.

DUT Code:

```
module Decoder_3x8 ( select, enable, out);

input wire[2:0] select;
input wire enable;
output wire[7:0] out;

assign out[0] = (enable & ~select[0] & ~select[1] & ~select[2]);
assign out[1] = (enable & ~select[0] & ~select[1] & select[2]);
assign out[2] = (enable & ~select[0] & select[1] & ~select[2]);
assign out[3] = (enable & ~select[0] & select[1] & select[2]);
assign out[4] = (enable & select[0] & ~select[1] & ~select[2]);
assign out[5] = (enable & select[0] & ~select[1] & select[2]);
assign out[6] = (enable & select[0] & select[1] & ~select[2]);
assign out[7] = (enable & select[0] & select[1] & select[2]);
endmodule;
```

Test Code:

```
module test_Decoder_3x8;

reg [2:0] select;
reg enable;
wire [7:0] out;

// Instantiate the 3x8 Decoder
Decoder_3x8 dut (
    .select(select),
    .enable(enable),
    .out(out)
);

// Clock generation (not used in this example)
reg clk = 0;
always #5 clk = ~clk;

// Testbench stimulus
initial begin
    // Test case 1
    select = 3'b000;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 2
    select = 3'b001;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 3
    select = 3'b010;
```

```

    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 4
    select = 3'b011;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 5
    select = 3'b100;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 6
    select = 3'b101;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);


    // Test case 7
    select = 3'b110;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 8
    select = 3'b111;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);
end

endmodule;

```

Output:

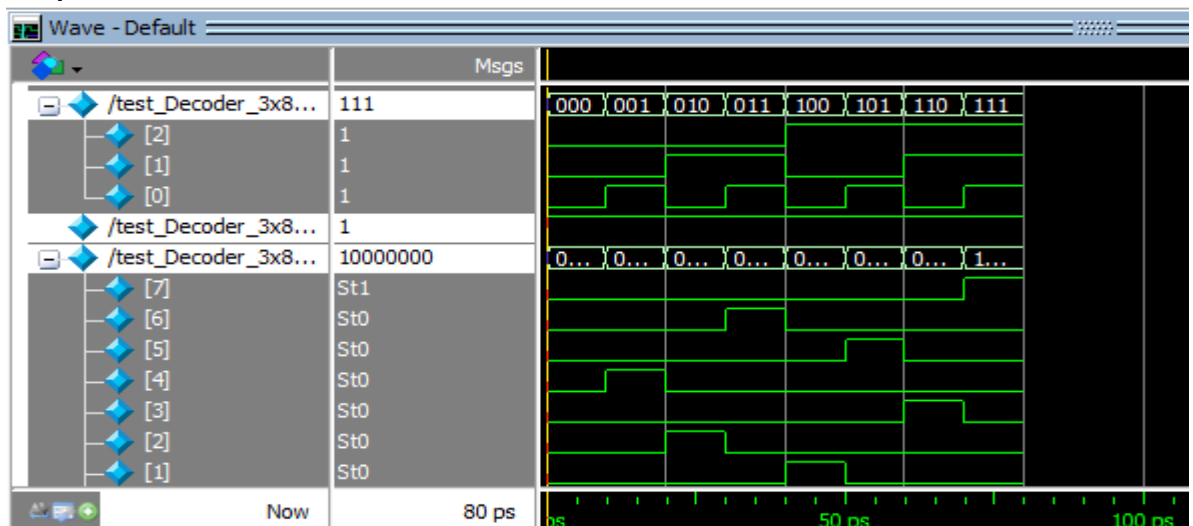

Task 3: Implement 3X8 Decoder using 2X4 Decoder.

DUT Code:

```
module Decoder_3x8_using_2x4 ( select, enable, out);

input wire[2:0] select;
input wire enable;
output wire[7:0] out;

wire [3:0] decoder1_out;
wire [3:0] decoder2_out;

Decoder_2x4 decoder1 (
    .select(select[1:0]),
    .enable(enable),
    .out(decoder1_out)
);

Decoder_2x4 decoder2 (
    .select(select[2:1]),
    .enable(enable),
    .out(decoder2_out)
);

assign out = {decoder2_out, decoder1_out};

endmodule;
```

Test Code:

```
module test_Decoder_3x8_using_2x4;

reg [2:0] select;
reg enable;
wire [7:0] out;

// Instantiate the 3x8 Decoder
Decoder_3x8_using_2x4 dut (
    .select(select),
    .enable(enable),
    .out(out)
);

// Clock generation (not used in this example)
reg clk = 0;
always #5 clk = ~clk;

// Testbench stimulus
initial begin
    // Test case 1
    select = 3'b000;
    enable = 1;
end
```

```
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 2
select = 3'b001;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 3
select = 3'b010;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 4
select = 3'b011;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);


// Test case 5
select = 3'b100;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 6
select = 3'b101;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 7
select = 3'b110;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

// Test case 8
select = 3'b111;
enable = 1;
#10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);
end
endmodule;
```


Output:

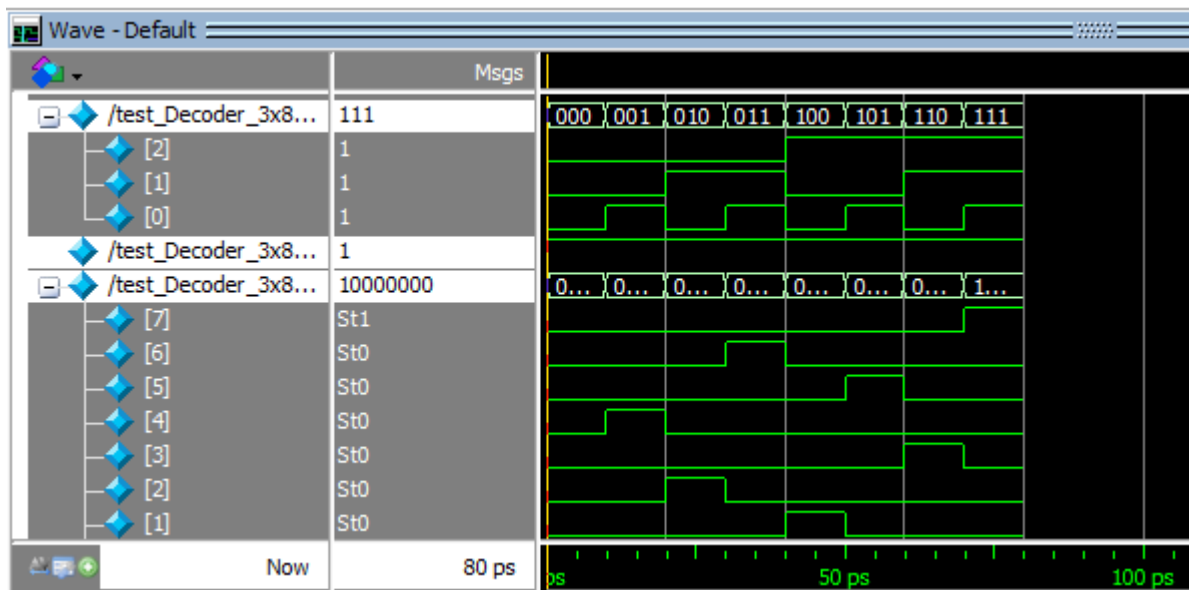

Task 4: Implement 4X16 Decoder using 3X8 Decoder.

DUT Code:

```
module Decoder_4x16_using_3x8 (select,enable,out);  
  
    input wire[3:0] select;  
    input wire enable;  
    output wire[15:0] out;  
  
    wire [7:0] decoder1_out;  
    wire [7:0] decoder2_out;  
  
    Decoder_3x8 decoder1 (  
        .select(select[2:0]),  
        .enable(enable),  
        .out(decoder1_out)  
    );  
  
    Decoder_3x8 decoder2 (  
        .select(select[3:1]),  
        .enable(enable),  
        .out(decoder2_out)  
    );  
  
    assign out = {decoder2_out, decoder1_out};  
  
endmodule;
```

Test Code:

```
module test_Decoder_4x16_using_3x8;
```

```

reg [3:0] select;
reg enable;
wire [15:0] out;

// Instantiate the 4x16 Decoder
Decoder_4x16_using_3x8 dut (
    .select(select),
    .enable(enable),
    .out(out)
);

// Clock generation (not used in this example)
reg clk = 0;
always #5 clk = ~clk;

// Testbench stimulus
initial begin
    // Test case 1
    select = 4'b0000;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 2
    select = 4'b0001;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);


    // Test case 3
    select = 4'b0010;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);

    // Test case 16
    select = 4'b1111;
    enable = 1;
    #10 $display("Input: select=%b, enable=%b, Output=%b", select,
enable, out);
end

endmodule;

```

Output:

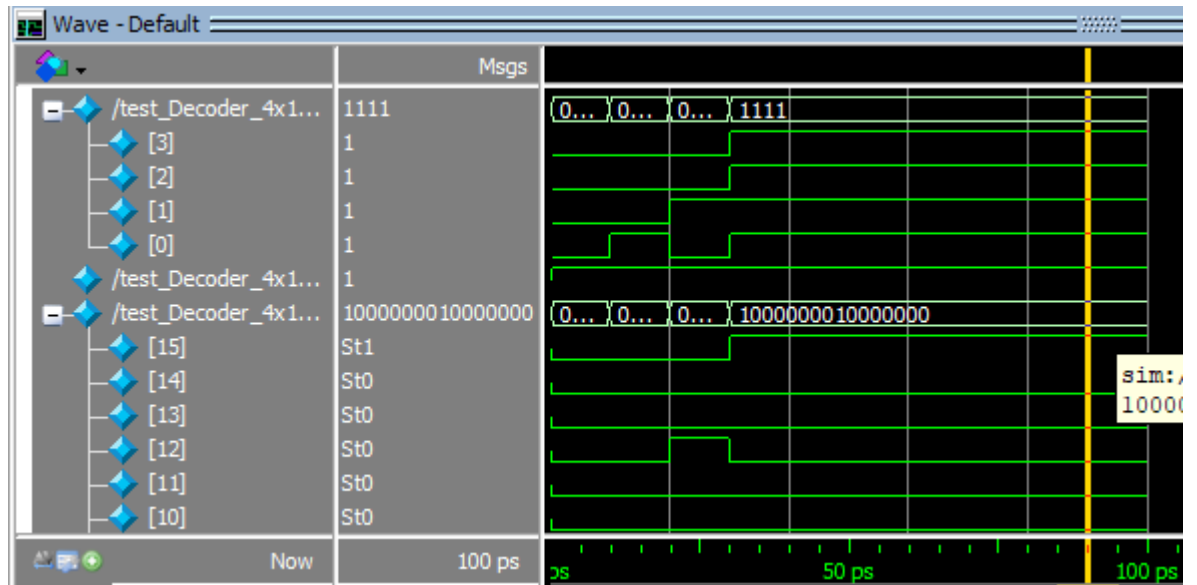

Reference:

To view my codes, please refer to my [GitHub Account](#).

Conclusion:

In conclusion, I have learned how to create and use decoders in Verilog.

The End.