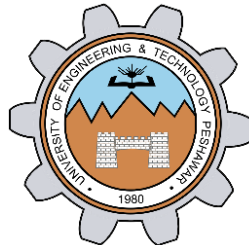


**COUNTERS IN
VERILOG**

LAB # 10



Fall 2023

CSE-304L


Computer Organization & Architecture Lab

Submitted by: **AIMAL KHAN**

Registration No.: **21PWCSE1996**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: 

Submitted to:

Dr. Bilal Habib

Monday, January 29, 2024

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown [Marks0] [Marks 0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
Total Marks Obtained: _____ Instructor Signature: _____				

Counters in Verilog

Objectives:

- Implement counters in Verilog
- Implement controlled and uncontrolled asynchronous counters
- Implement RAM

Tasks:

Task 1: Write a Verilog code to implement 4-bit counter

DUT Code:

```
module Counter_4_bit(  
    input wire clock,  
    input wire reset,  
    output reg [3:0] count  
);  
    always @(posedge clock or posedge reset)  
    begin  
        if(reset) begin  
            count <= 4'b0000;  
        end else begin  
            count <= count +1;  
        end  
    end  
endmodule
```

Test Code:

```
module test_Counter_4_bit();  
    reg clk;  
    reg rst;  
    wire [3:0] count;  
  
    Counter_4_bit counter(  
        .clock(clk),  
        .reset(rst),  
        .count(count)  
    );  
  
    always begin  
        #5  
        clk = ~clk;  
    end  
  
    initial begin  
        clk = 0;  
    end  
endmodule
```

```

rst = 0;


// Reset the counter initially
rst = 1;
#10 rst = 0;
#20;

$display("Time = 0, Count = %b", count);
#10;
$display("Time = 10, Count = %b", count);
#10;
$display("Time = 20, Count = %b", count);
#10;
$display("Time = 30, Count = %b", count);

end
endmodule

```

Output:

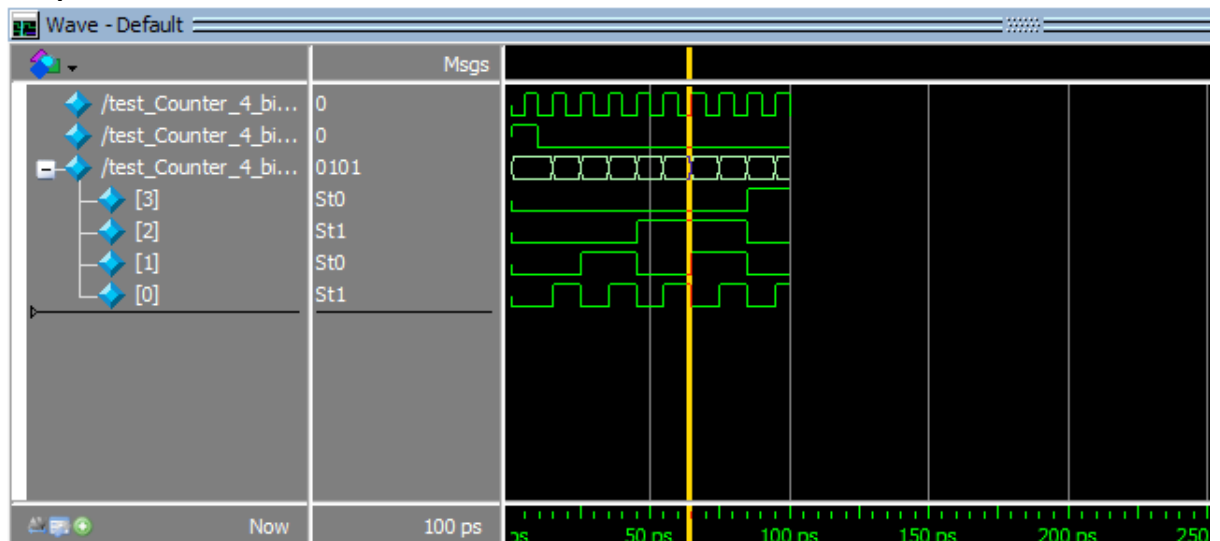

Task 2: Write a Verilog code to implement 8-bit counter

DUT Code:

```

module Counter_8_bit(
    input wire clock,
    input wire reset,
    output reg [7:0] count
);

always @(posedge clock or posedge reset)
begin
    if(reset)
        count <= 8'b00000000;
    else
        count <= count +1;
end
endmodule

```

Test Code:

```
module test_Counter_8_bit();
    reg clk;
    reg rst;
    wire [7:0] count;

    Counter_8_bit counter(
        clk, rst, count
    );

    always begin
        #5 clk = ~clk;
    end

    initial begin
        clk = 0;
        rst = 0;


        rst = 1;
        #10 rst = 0;

        #20;
        $display("Time = 0, Count = %b", count);
        #10;
        $display("Time = 10, Count = %b", count);
        #10;
        $display("Time = 20, Count = %b", count);
        #10;
        $display("Time = 30, Count = %b", count);


        #10;
        $display("Time = 30, Count = %b", count);
        #10;
        $display("Time = 30, Count = %b", count);
        #10;
        $display("Time = 30, Count = %b", count);
        #10;
        $display("Time = 30, Count = %b", count);

    end
endmodule
```


Output:

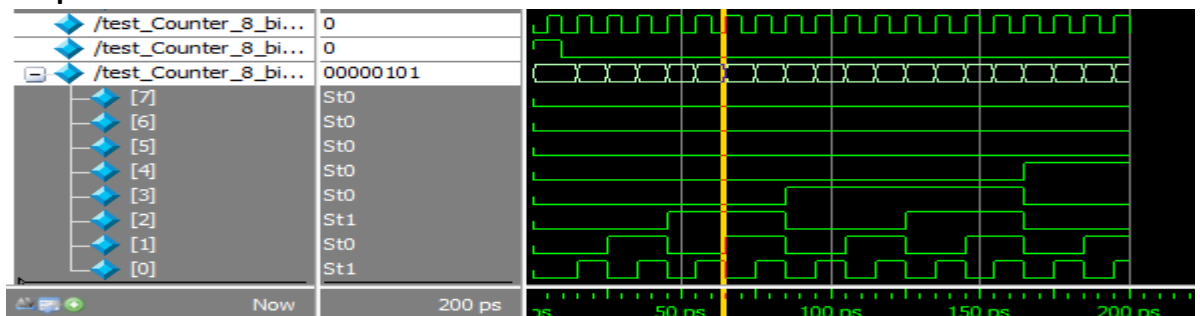

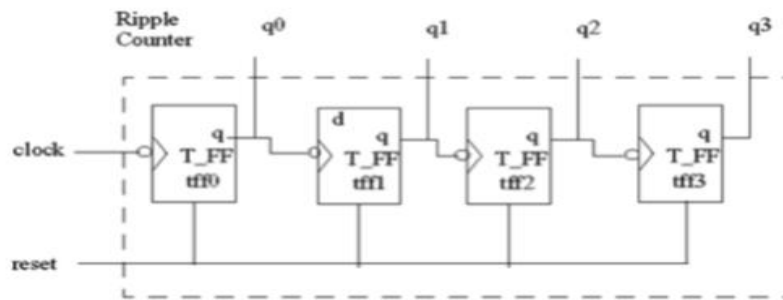Task 3: Implement 4 BIT Uncontrolled Asynchronous UP COUNTER in Verilog using T FLIP FLOP.



Block Diagram

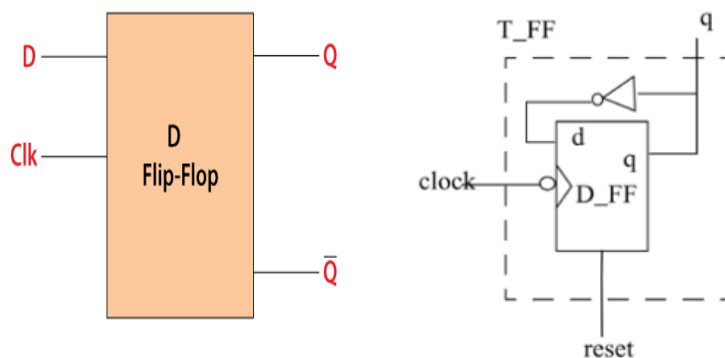

Circuit Diagram

DUT Code:

```
module T_Uncontrolled_Async_Counter_4_bit(
    input wire clock,
    input wire reset,
    output reg [3:0] count
);
    reg [3:0] t_signals;

    always @(posedge clock or posedge reset) begin
        if (reset) begin
            t_signals <= 4'b0000; // Reset T signals to 0 when reset
            is high
        end else begin
            t_signals <= t_signals + 1; // Increment T signals on
            each clock cycle
        end
    end

    T_Flip_Flop tff0 (.T(t_signals[0]), .clock(clock),
        .Q(count[0]));
    T_Flip_Flop tff1 (.T(t_signals[1]), .clock(clock),
        .Q(count[1]));
```

```

        T_Flip_Flop tff2 (.T(t_signals[2]), .clock(clock),
        .Q(count[2]));
        T_Flip_Flop tff3 (.T(t_signals[3]), .clock(clock),
        .Q(count[3]));

endmodule

```

Test Code:

```

module test_T_Uncontrolled_Async_Counter_4_bit();
    reg clk;
    reg rst;
    wire [3:0] count;

    T_Uncontrolled_Async_Counter_4_bit uut (
        .clock(clk),
        .reset(rst),
        .count(count)
    );

    always begin
        #5 clk = ~clk;
    end

    // Testbench initialization
    initial begin
        clk = 0;
        rst = 0;


        // Reset the counter initially
        rst = 1;
        #10 rst = 0;

        // Wait for some clock cycles and observe the counter
        #20;


        $display("Time = 0, Count = %b", count);
        #10;
        $display("Time = 10, Count = %b", count);
        #10;
        $display("Time = 20, Count = %b", count);
        #10;
        $display("Time = 30, Count = %b", count);
    end
endmodule;

```

Output:

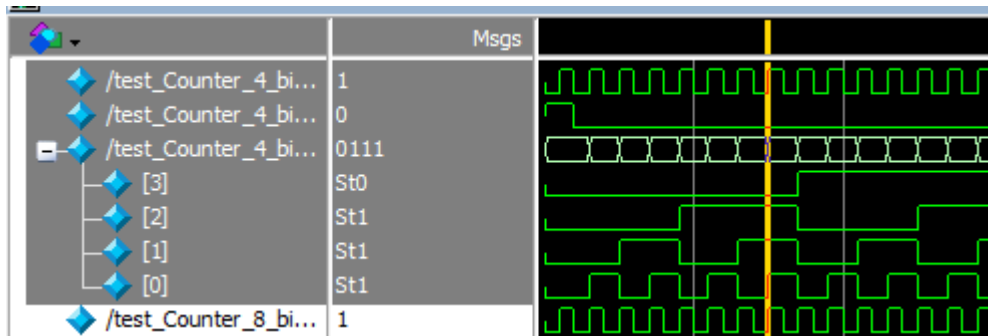

 Task 4: Implement 4 BIT Controlled Asynchronous UP COUNTER in Verilog using T FLIP FLOP.



DUT Code:

```
module T_Controlled_Async_Counter_4_bit(
    input wire clock,
    input wire reset,
    input wire enable,
    output reg [3:0] count
);
    reg [3:0] t_signals;

    always @(posedge clock or posedge reset) begin
        if (reset) begin
            t_signals <= 4'b0000; // Reset T signals to 0 when reset
            is high
        end else if (enable) begin
            t_signals <= t_signals + 1; // Increment T signals on
            each clock cycle when enable is high
        end
    end

    T_Flip_Flop tff0 (.T(t_signals[0]), .clock(clock),
        .Q(count[0]));
    T_Flip_Flop tff1 (.T(t_signals[1]), .clock(clock),
        .Q(count[1]));
```



```

        T_Flip_Flop tff2 (.T(t_signals[2]), .clock(clock),
        .Q(count[2]));
        T_Flip_Flop tff3 (.T(t_signals[3]), .clock(clock),
        .Q(count[3]));

endmodule

```

Test Code:

```

module test_T_Controlled_Async_Counter_4_bit();
reg clk;
reg rst;
reg enable;
wire [3:0] count;

// Instantiate the controlled asynchronous up-counter module
T_Controlled_Async_Counter_4_bit uut (
    .clock(clk),
    .reset(rst),
    .enable(enable),
    .count(count)
);

// Clock generation
always begin
    #5 clk = ~clk; // Toggle the clock every 5 time units
end

// Testbench initialization
initial begin
    clk = 0;
    rst = 0;
    enable = 1; // Enable the counter

    // Reset the counter initially
    rst = 1;
    #10 rst = 0;


    // Wait for some clock cycles and observe the counter
    #20;

    // Test the counter for several clock cycles
    $display("Time = 0, Count = %b", count);
    #10;
    $display("Time = 10, Count = %b", count);
    #10;
    $display("Time = 20, Count = %b", count);
    #10;
    $display("Time = 30, Count = %b", count);

    // Finish simulation
    $finish;
end
endmodule

```

Output:

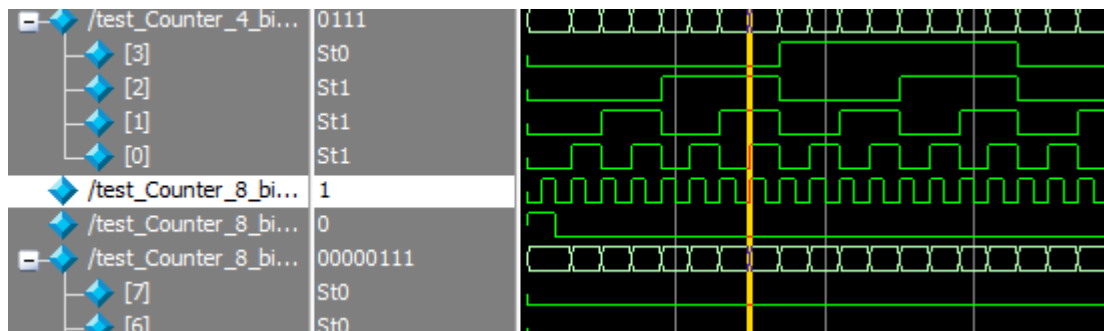

Task 5: Implement 16x8 RAM in Verilog.

DUT Code:

```
module RAM_16x8 (clk, addr, data_in, write_enable, data_out);
    input wire clk;
    input wire [3:0] addr;
    input wire [7:0] data_in;
    input wire write_enable;
    output wire [7:0] data_out;

    reg [7:0] memory [0:15]; // 16 words by 8 bits

    // Read operation
    assign data_out = (write_enable) ? 8'bzzzz_zzzz : memory[addr];

    // Write operation
    always @(posedge clk) begin
        if (write_enable)
            memory[addr] <= data_in;
    end
endmodule
```

Test Code:

```
// Testbench for 16x8 RAM
module test_RAM_16x8;

    // Inputs
    reg clk;
    reg [3:0] addr;
    reg [7:0] data_in;
    reg write_enable;

    // Outputs
    wire [7:0] data_out;

    // Instantiate the RAM module
    ram_16x8 uut (
        .clk(clk),
```

```

        .addr(addr),
        .data_in(data_in),
        .write_enable(write_enable),
        .data_out(data_out)
    );

    // Clock generation
    always begin
        #5 clk = ~clk;
    end

    // Initial block
    initial begin
        // Initialize inputs
        clk = 0;
        addr = 4'b0000;
        data_in = 8'b0000_0000;
        write_enable = 0;

        // Apply write operation to store data
        addr = 4'b0001;
        data_in = 8'b1010_1010;
        write_enable = 1;
        #10 write_enable = 0;

        // Read from the RAM
        addr = 4'b0001;
        write_enable = 0;


        // Monitor signals
        $monitor("Time=%t, clk=%b, addr=%b, data_in=%b, write_enable=%b,
        data_out=%b", $time, clk, addr, data_in, write_enable, data_out);

        // Run simulation for 100 clock cycles
        #100 $finish;
    end

endmodule

```

Output:

 

```
ModelSim> vsim -gui work.test_RAM_16x8
# vsim -gui work.test_RAM_16x8
# Start time: 22:22:54 on Jan 31, 2024
# Loading work.test_RAM_16x8
# Loading work.ram_16x8
add wave -position insertpoint sim:/test_RAM_16x8/*
VSIM 3> run
# Time=          10, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          15, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          20, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          25, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          30, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          35, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          40, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          45, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          50, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          55, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          60, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          65, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          70, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          75, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          80, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          85, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          90, clk=0, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
# Time=          95, clk=1, addr=0001, data_in=10101010, write_enable=0, data_out=10101010
```

Reference:

To view my codes, please refer to my [GitHub Account](#).

Conclusion:

In summary of this lab, I have learned how to implement simple counters, controlled and uncontrolled asynchronous T counters. I also learned how to implement RAM in Verilog. This lab will help in my future endeavors.

The End.