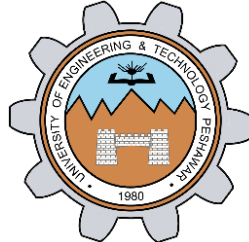


**INTRODUCTION TO
VERILOG**

LAB # 06



Fall 2023

CSE-304L

Computer Organization & Architecture Lab

Submitted by: **AIMAL KHAN**

Registration No.: **21PWCSE1996**

Class Section: **A**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

A handwritten signature in black ink, appearing to be "Aimal Khan", written over a horizontal line.

Submitted to:

Dr. Bilal Habib

Friday, November 10, 2023

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

ASSESSMENT RUBRICS COA LABS

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
1. Objectives of Lab	All objectives of lab are properly covered [Marks 10]	Objectives of lab are partially covered [Marks 5]	Objectives of lab are not shown [Marks 0]	
2. MIPS instructions with Comments and proper indentations.	All the instructions are well written with comments explaining the code and properly indented [Marks 20]	Some instructions are missing are poorly commented code [Marks 10]	The instructions are not properly written [Marks 0]	
3. Simulation run without error and warnings	The code is running in the simulator without any error and warnings [Marks 10]	The code is running but with some warnings or errors. [Marks 5]	The code is written but not running due to errors [Marks 0]	
4. Procedure	All the instructions are written with proper procedure [Marks 20]	Some steps are missing [Marks 10]	steps are totally missing [Marks 0]	
5. OUTPUT	Proper output of the code written in assembly [Marks 20]	Some of the outputs are missing [Marks 10]	No or wrong output [Marks 0]	
6. Conclusion	Conclusion about the lab is shown and written [Marks 20]	Conclusion about the lab is partially shown [Marks 10]	Conclusion about the lab is not shown [Marks0] [Marks 0]	
7. Cheating			Any kind of cheating will lead to 0 Marks	
Total Marks Obtained: _____ Instructor Signature: _____				


Introduction to Verilog

Objectives:

- Introduction to Verilog
- Introduction to hardware design, Model Sim and testing the hardware design.

Tasks:

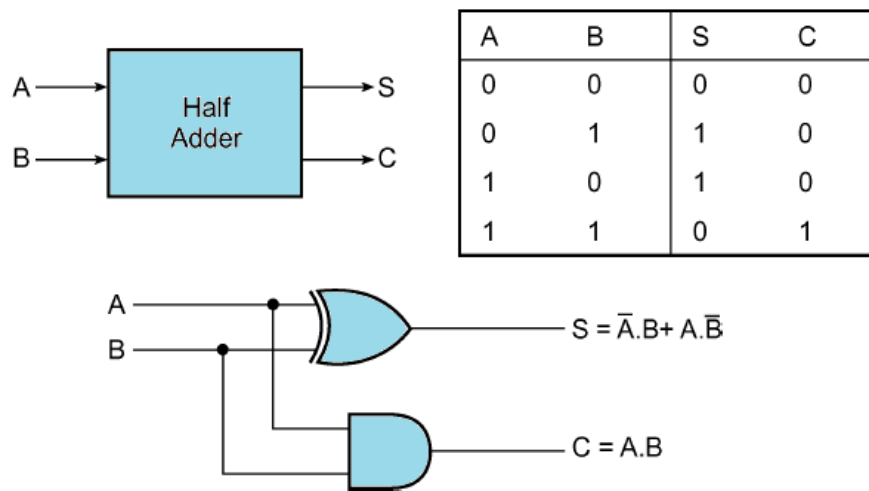Task 1: Implement half adder in Verilog using gate level modeling.



DUT Code:

```
module HalfAdder(input1, input2, sum, carry);  
  
    input input1, input2;  
    output sum, carry;  
  
    xor xorGate(sum, input1, input2);  
    and andGate(carry, input1, input2);  
  
endmodule;
```

Test Code:

```
module simulateHalfAdder();  
    reg input1, input2;  
    wire sum, carry;  
  
    HalfAdder ha(input1, input2, sum, carry);  
  
    initial  
    begin  
        $display("I1, I2, Sum, Carry");  
    end  
endmodule;
```

```

input1 = 0;
input2 = 0;
#10
$display("%b, %b, %b, %b", input1, input2, sum, carry);

input1 = 0;
input2 = 1;
#10
$display("%b, %b, %b, %b", input1, input2, sum, carry);


input1 = 1;
input2 = 0;
#10
$display("%b, %b, %b, %b", input1, input2, sum, carry);

input1 = 1;
input2 = 1;
#10
$display("%b, %b, %b, %b", input1, input2, sum, carry);


end
endmodule;

```

Output:

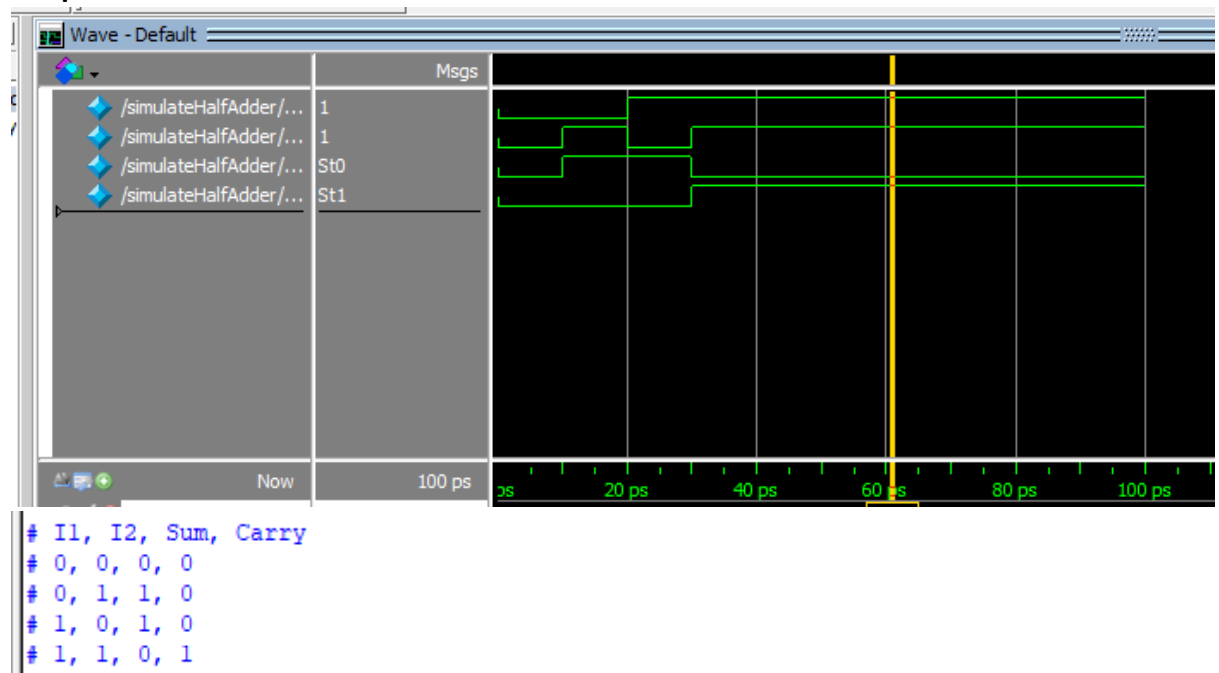

 Task 2: Implement full adder using two half adder. (use the above half adder to create full adder)



DUT Code:

```
module FullAdder(input1, input2, carryIn, sum, carryOut);
input input1, input2, carryIn;
output sum, carryOut;

wire sum1, carry1, carry2;

HalfAdder ha1(input1, input2, sum1, carry1);
HalfAdder ha2(carryIn, sum1, sum, carry2);

or orGate(carryOut, carry1, carry2);

endmodule;
```

Test Code:

```
module simulateFullAdder();
reg input1, input2, carryIn;

wire sum, carryOut;
FullAdder fa(input1, input2, carryIn, sum, carryOut);

initial
begin
$display("I1, I2, Cin, Sum, Cout");

input1 = 0;
input2 = 0;
carryIn = 0;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

input1 = 1;
input2 = 0;
carryIn = 0;
#10
```

```
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

input1 = 0;
input2 = 1;
carryIn = 0;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

input1 = 1;
input2 = 1;
carryIn = 0;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

input1 = 0;
input2 = 0;
carryIn = 1;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);


input1 = 1;
input2 = 0;
carryIn = 1;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

input1 = 0;
input2 = 1;
carryIn = 1;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);


input1 = 1;
input2 = 1;
carryIn = 1;
#10
$display("%b, %b, %b, %b, %b", input1, input2, carryIn, sum,
carryOut);

end
endmodule
```

Output:

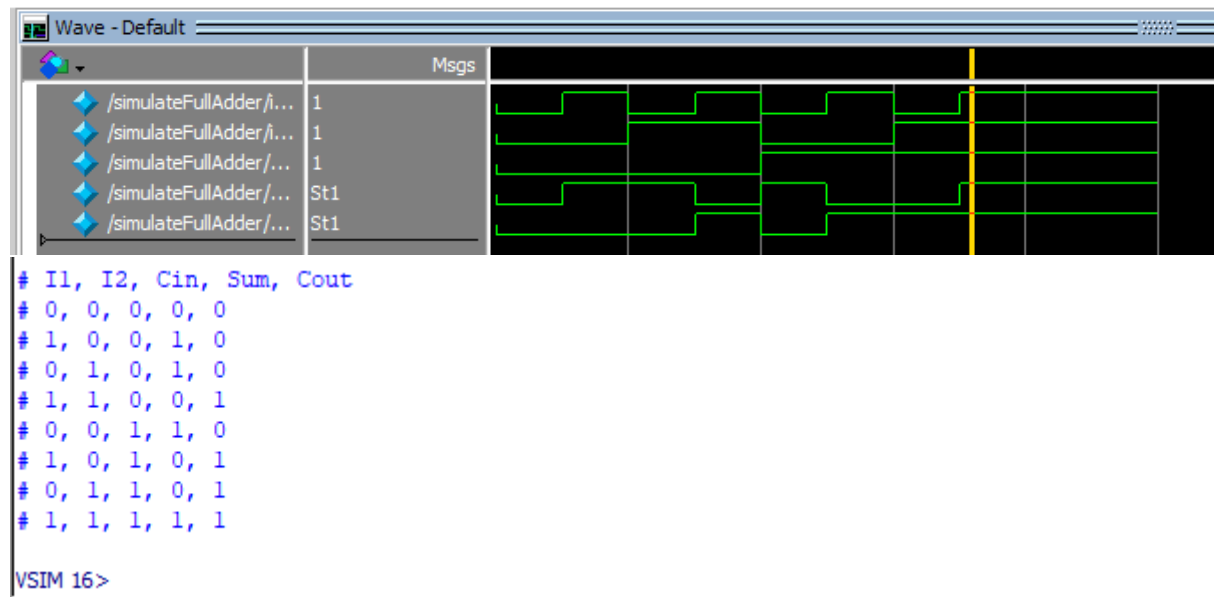

 Task 3: Write a Verilog code for 4 bit ripple carry adder.



4-bit Ripple Carry Adder

DUT Code:

```
module FourBitAdder(A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);  
  
    input A0, B0, A1, B1, A2, B2, A3, B3, Cin;  
    output S0, S1, S2, S3, Cout;  
  
    wire C0, C1, C2;  
  
    FullAdder faA(A0, B0, Cin, S0, C0);
```

```
FullAdder faB(A1, B1, C0, S1, C1);
FullAdder faC(A2, B2, C1, S2, C2);
FullAdder faD(A3, B3, C2, S3, Cout);

endmodule;
```

Test Code:

```
module simulateFourBitAdder();

reg A0, B0, A1, B1, A2, B2, A3, B3, Cin;
wire S0, S1, S2, S3, Cout;

FourBitAdder fba(A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2,
S3, Cout);

initial
begin
$display("A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3,
Cout");

Cin = 0;
A0 = 0;
B0 = 0;
A1 = 0;
B1 = 0;
A2 = 0;
B2 = 0;
A3 = 0;
B3 = 0;
#10
$display("%b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b",
A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);

Cin = 1;
A0 = 0;
B0 = 0;
A1 = 0;
B1 = 0;
A2 = 0;
B2 = 1;
A3 = 0;
B3 = 0;
#10
$display("%b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b",
A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);

Cin = 1;
A0 = 1;
B0 = 0;
A1 = 1;
B1 = 0;
A2 = 1;
B2 = 0;
```



```

A3 = 1;
B3 = 0;
#10
$display("%b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b",
A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);


Cin = 0;
A0 = 1;
B0 = 1;
A1 = 1;
B1 = 0;
A2 = 1;
B2 = 1;
A3 = 1;
B3 = 0;
#10
$display("%b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b",
A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);

Cin = 0;
A0 = 0;
B0 = 0;
A1 = 1;
B1 = 1;
A2 = 1;
B2 = 0;
A3 = 1;
B3 = 1;
#10
$display("%b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b, %b",
A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout);

end
endmodule;

```

Output:

 

```
VSIM 44> run
# A0, B0, A1, B1, A2, B2, A3, B3, Cin, S0, S1, S2, S3, Cout
# 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0, 0
# 0, 0, 0, 0, 0, 1, 0, 0, 1, 1, 0, 1, 0, 0
# 1, 0, 1, 0, 1, 0, 1, 0, 1, 0, 0, 0, 0, 1
# 1, 1, 1, 0, 1, 1, 1, 0, 0, 0, 0, 1, 0, 1
# 0, 0, 1, 1, 1, 1, 0, 1, 1, 0, 0, 0, 1, 1
```

Reference:

To view my codes, please refer to my [GitHub Account](#).

Conclusion:

In conclusion, I have learnt the basic of Verilog, model Sim, designing of hardware and the testing the hardware for its functionality. I can now create my own piece of hardware from basic gates and then use my hardware in designing other hardware components.

The End.